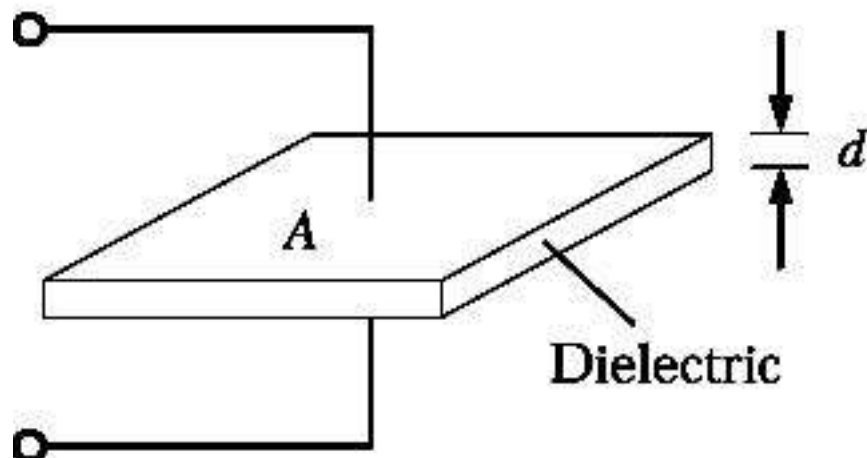



CONDENSADORES E BOBINES

DISPOSITIVOS PASSIVOS DE ARMAZENAMENTO DE ENERGIA

CONDENSADOR





Basic parallel-plates capacitor

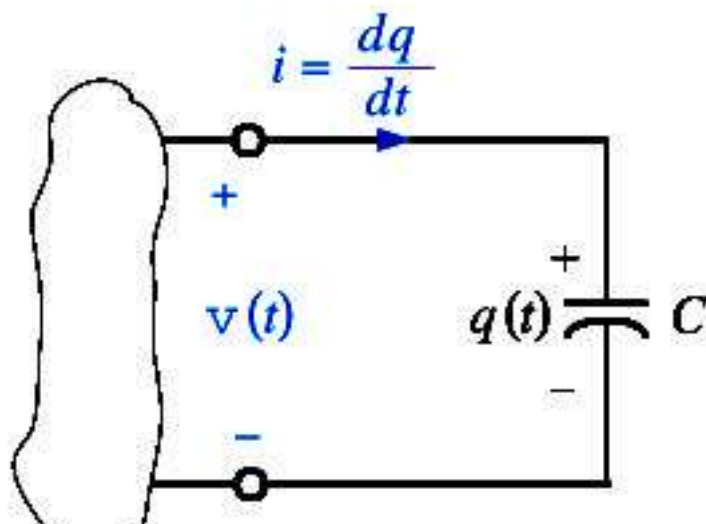



CIRCUIT REPRESENTATION

CONVENÇÃO PASSIVA PARA A CORRENTE

Typical Capacitors

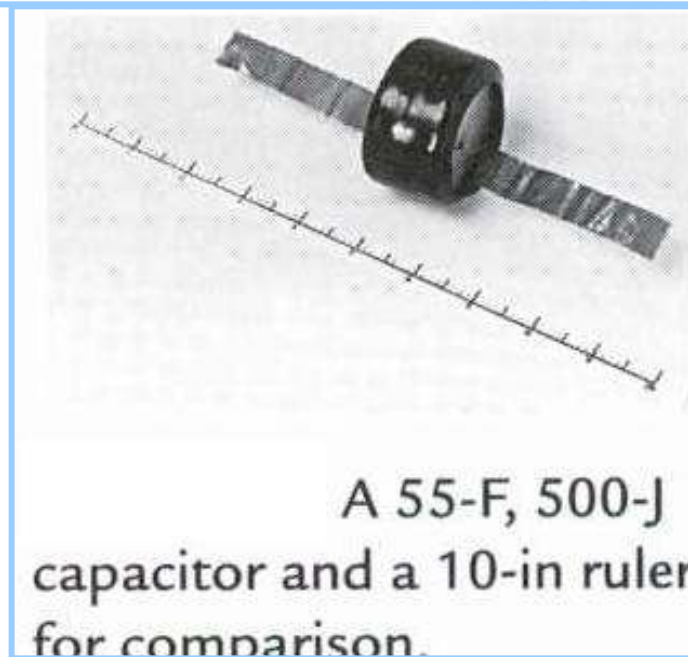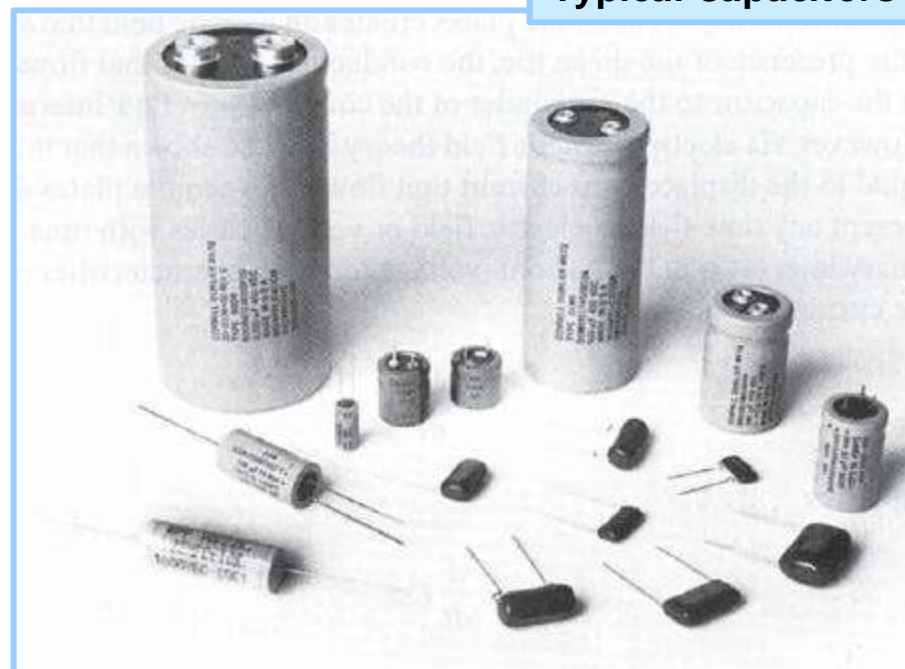

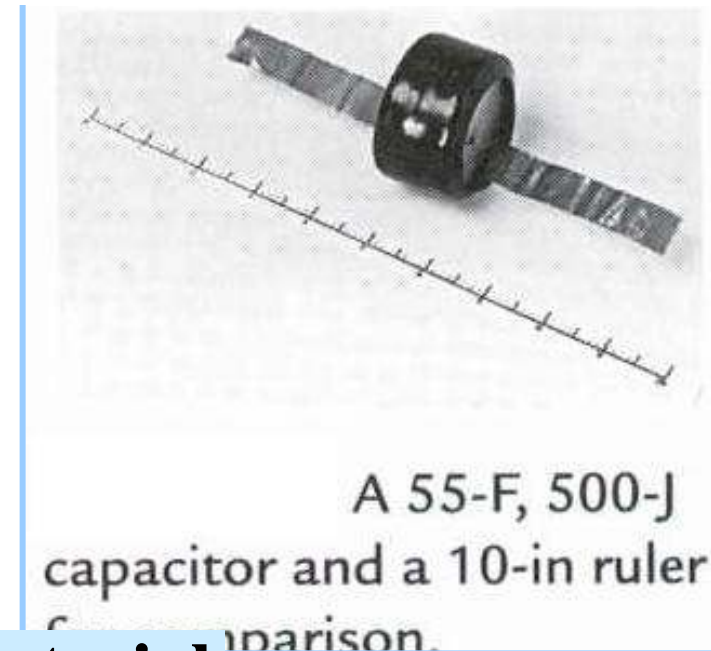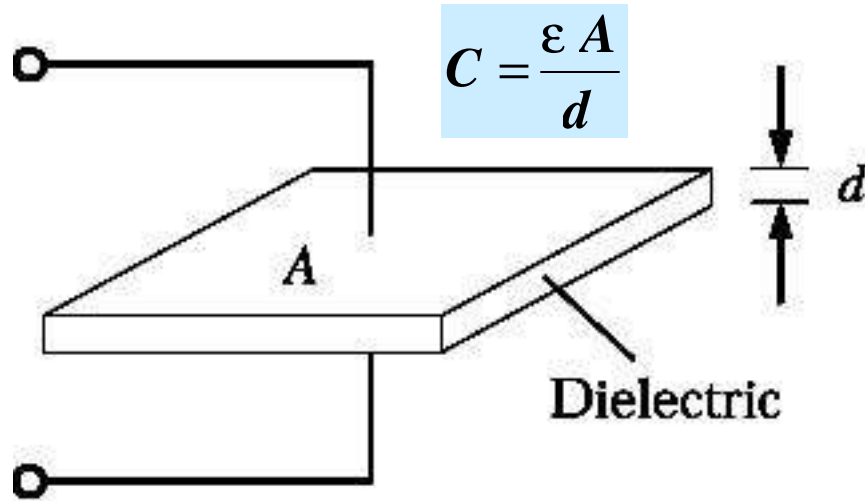A 55-F, 500-J capacitor and a 10-in ruler for comparison.



ϵ Constante dielectrica do material

$$55F = \frac{8.85 \times 10^{-12} A}{1.016 \times 10^{-4}} \Rightarrow A = 6.3141 \times 10^8 m^2$$

Valores de capacidade são baixos. Microfarads é típico
Circuitos integrados é ainda mais baixo ... pico farads é típico

Condensadores obedecem
À Lei de Coulomb :


C é a capacidade do condensador

carga
tensão el.

Um Farad(F) é a capacidade de um dispositivo
Que armazena um coulomb de carga a um volt.

$$\text{Farad} = \frac{\text{Coulomb}}{\text{Volt}}$$

$$Q = CV_C$$

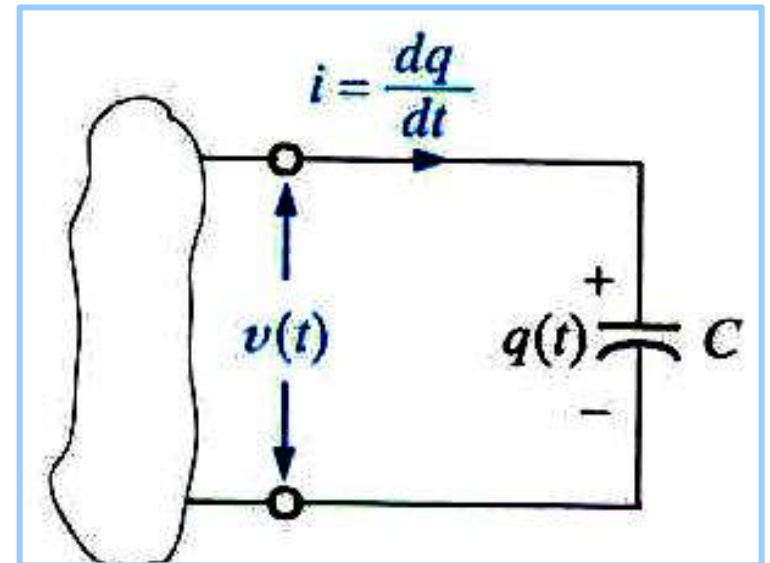

Representação do elem. circuito


EXAMPLE Queda de tensão de um cond. De 2 micro
Farads que armazene 10mC de carga

$$V_C = \frac{1}{C} Q = \frac{1}{2 * 10^{-6}} 10 * 10^{-3} = 5000 \text{ v}$$

Capacitance in Farads, charge in Coulombs
result in voltage in Volts

CONDENSADORES PODEM SER PERIGOSOS!!!!!!!!!!

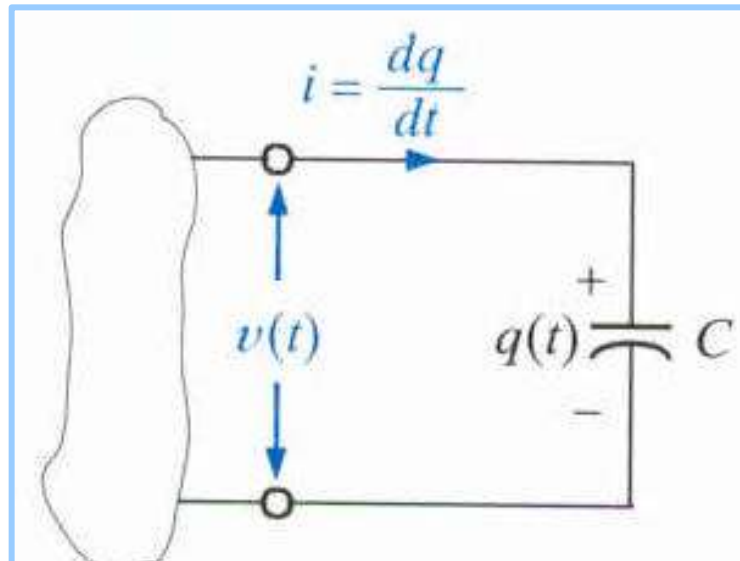Condensadores apenas armazenam e libertam carga.
NÃO “CRIAM” CARGA.



Linear capacitor circuit representation

$$i(t) = C \frac{dv}{dt}(t)$$

$$Q_C = CV_C$$

LEI DA CAPACIDADE!

**Se a tensão varia a carga varia e portanto há uma corrente
Que flui.....**

**Podemos exprimir a tensão em função
Da corrente.**

$$V_C(t) = \frac{1}{C} Q = \frac{1}{C} \int_{-\infty}^t i_C(x) dx$$

Forma integral .

Uma consequência é que ...

$$V_C(t-) = V_C(t+); \forall t$$

**Tensão aos terminais do condensador
TEM QUE SER CONTÍNUA.**

**... Ou a corrente em função da tensão
Aos seus terminais**

$$i_C = \frac{dQ}{dt} = C \frac{dV_C}{dt}$$

Forma diferencial da lei da capacitância


E daí ??

$$V_C = Const \Rightarrow i_C = 0$$

Comportamento estacionário ou DC

**Se a tensão é constante o condensador
COMPORTA-SE COMO UM CIRCUITO
ABERTO.**

Condensador como elemento de circuito

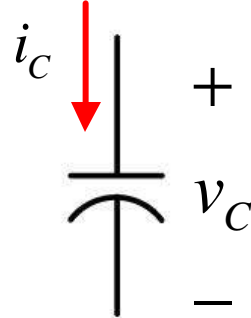

$$i_C(t) = C \frac{dv_C}{dt}(t)$$

$$i_R = \frac{1}{R} v_R$$

$$v_C(t) = \frac{1}{C} \int_{-\infty}^t i_C(x) dx$$

$$v_R = R i_R$$

Ohm's Law


$$\int_{-\infty}^t = \int_{-\infty}^{t_0} + \int_{t_0}^t$$

$v_C(t_0)$

$$v_C(t) = \frac{1}{C} \int_{-\infty}^{t_0} i_C(x) dx + \frac{1}{C} \int_{t_0}^t i_C(x) dx$$

$$v_C(t) = v_C(t_0) + \frac{1}{C} \int_{t_0}^t i_C(x) dx$$

Condensador como armazenador de energia

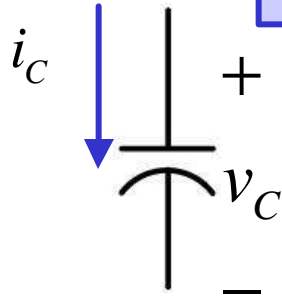

Potência instantânea

W

$$p_C(t) = v_C(t)i_C(t)$$

$$i_C(t) = C \frac{dv_C}{dt}(t)$$

$$p_C(t) = C v_C(t) \frac{dv_C}{dt}$$

$$p_C(t) = C \frac{d}{dt} \left(\frac{1}{2} v_C^2(t) \right)$$

Energia é integral da potência

$$w_C(t_2, t_1) = \int_{t_1}^{t_2} p_C(x) dx$$


$$p_C(t) = \frac{1}{C} \frac{d}{dt} \left(\frac{1}{2} q_C^2(t) \right)$$

Se t_1 é menos infinito temos
“energia armazenada em t_2 .”

Se ambos os limites são infinitos temos
A energia total armazenada.

$$w_C(t_2, t_1) = \frac{1}{2} C v_C^2(t_2) - \frac{1}{2} C v_C^2(t_1)$$
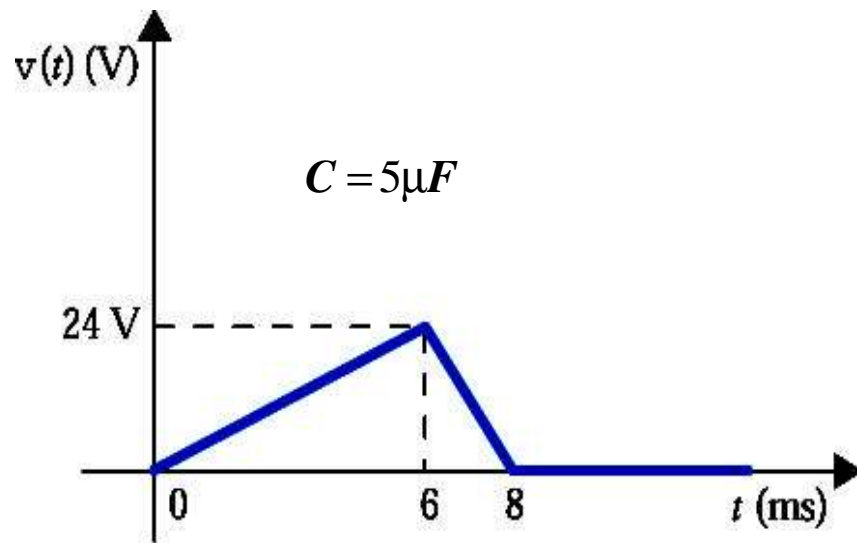
$$w_C(t_2, t_1) = \frac{1}{C} q_C^2(t_2) - \frac{1}{C} q_C^2(t_1)$$



Exemplo

Energia armazenada de 0 - 6 msec

$$w_C(0,6) = \frac{1}{2} C v_C^2(6) - \frac{1}{2} C v_C^2(0)$$

$$w_C(0,6) = \frac{1}{2} 5 * 10^{-6} [F] * (24)^2 [V^2]$$

Carga armazenada aos 3msec

$$q_C(3) = C v_C(3)$$



$$q_C(3) = 5 * 10^{-6} [F] * 12 [V] = 60 \mu\text{C}$$

“energia total armazenada?”

“carga total armazenada?” ...

BOBINES

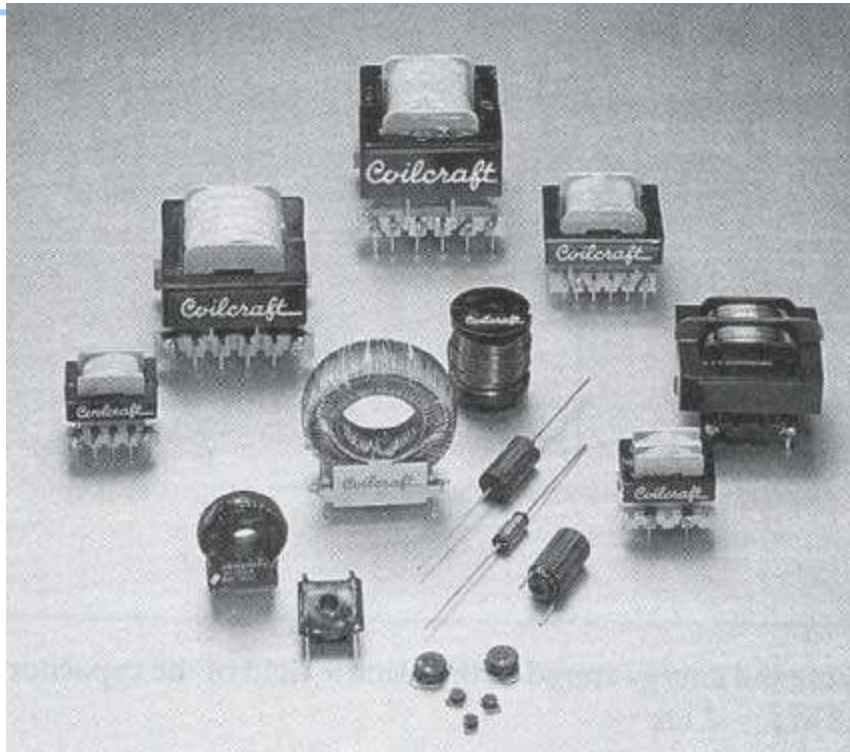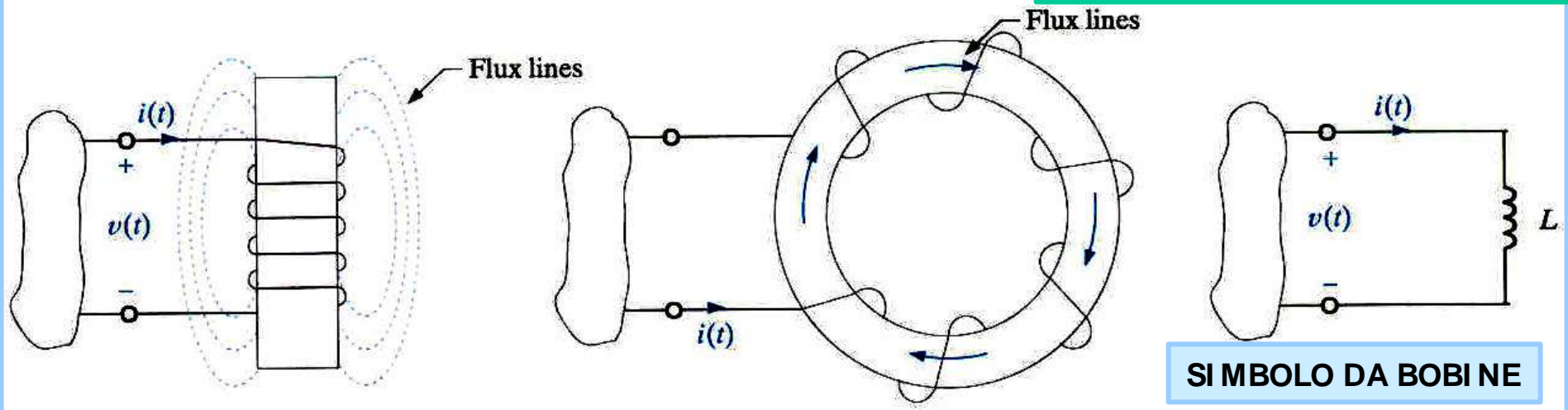**ATENÇÃO À CONVENÇÃO
PARA TENSÃO E CORRENTE**



**Um fluxo variável no tempo
Induz um campo electro-
-magnético, surgindo uma
Tensão (induzida) aos
Terminais da bobine.**

FLUXO MAGNÉTICO VARIÁVEL NO TEMPO
INDUZ UMA TENSÃO NA BOBINE

$$v_L = \frac{d\phi}{dt}$$

Lei da indução

Para uma bobine “normal” (linear), o fluxo é
Proporcional à corrente.


$$\phi = Li_L \Rightarrow v_L = L \frac{di_L}{dt}$$

A CONSTANTE DE PROPORCIONALIDADE L CHAMA-
-SE INDUTÂNCIA


A INDUTÂNCIA MEDE-SE EM HENRY

$$\text{HENRY} = \frac{\text{Volt}}{\text{Amp} / \text{sec}}$$

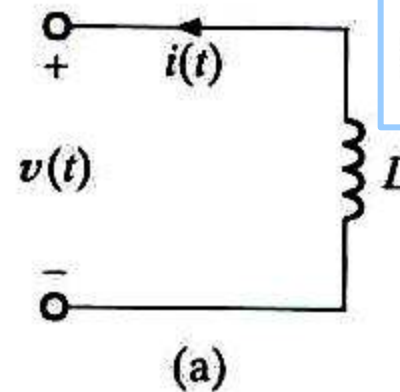
Write the i - v
relationship for the
following inductors.



$$v(t) = -L \frac{di(t)}{dt}$$

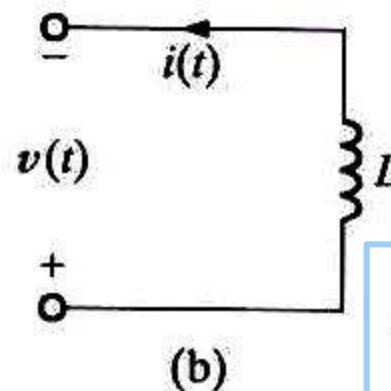

$$v(t) = L \frac{di(t)}{dt}$$

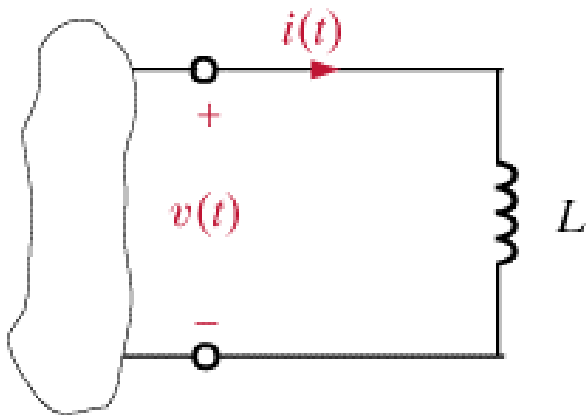

$$v_L = L \frac{di_L}{dt}$$

Differential form of induction law

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(x) dx$$

Integral form of induction law

$$i_L(t) = i_L(t_0) + \frac{1}{L} \int_{t_0}^t v_L(x) dx; \quad t \geq t_0$$

Conseq. Directa da forma integral...

$$i_L(t-) = i_L(t+); \quad \forall t$$

A corrente tem que ser contínua...

Outra consequência

$$i_L = \text{Const.} \Rightarrow v_L = 0$$

Comportamento DC

Potência e energia armazenada

$$p_L(t) = v_L(t) i_L(t) \quad \text{W}$$

$$p_L(t) = L \frac{di_L}{dt}(t) i_L(t) = \frac{d}{dt} \left(\frac{1}{2} L i_L^2(t) \right)$$

$$w_L(t_2, t_1) = \int_{t_1}^{t_2} \frac{d}{dt} \left(\frac{1}{2} L i_L^2(x) \right) dx \quad \text{J}$$

Current in Amps, Inductance in Henrys
yield energy in Joules

$$w(t_2, t_1) = \frac{1}{2} L i_L^2(t_2) - \frac{1}{2} L i_L^2(t_1)$$


Energy stored on the interval
Can be positive or negative

$$w_L(t) = \frac{1}{2} L i_L^2(t)$$

“Energy stored at time t”
Must be non-negative.
Passive element!!!

LEARNING EXAMPLE

L=10mH. FIND THE VOLTAGE

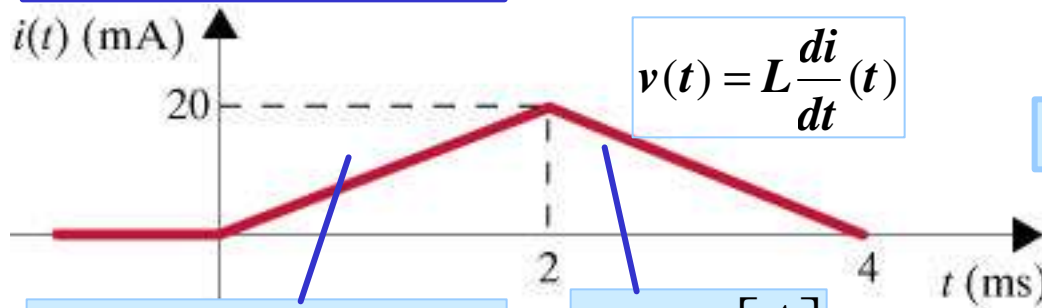


$$m = \frac{20 \times 10^{-3} \text{ A}}{2 \times 10^{-3} \text{ s}} = 10 \left[\frac{\text{A}}{\text{s}} \right]$$

$$m = -10 \left[\frac{\text{A}}{\text{s}} \right]$$

THE DERIVATIVE OF A STRAIGHT LINE IS ITS SLOPE

$$\frac{di}{dt} = \begin{cases} 10(\text{A/s}) & 0 \leq t \leq 2\text{ms} \\ -10(\text{A/s}) & 2 < t \leq 4\text{ms} \\ 0 & \text{elsewhere} \end{cases}$$
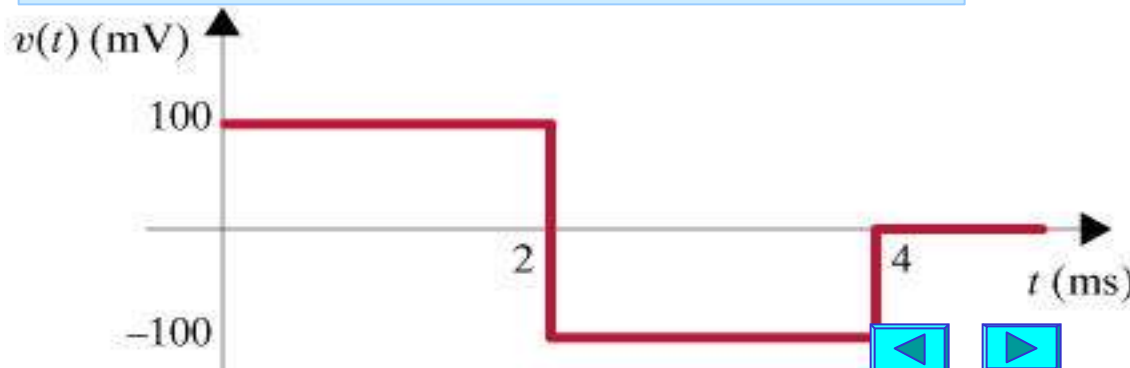
$$\left. \begin{array}{l} \frac{di}{dt}(t) = 10(\text{A/s}) \\ L = 10 \times 10^{-3} \text{ H} \end{array} \right\} \Rightarrow v(t) = 100 \times 10^{-3} \text{ V} = 100 \text{ mV}$$



ENERGY STORED BETWEEN 2 AND 4 ms

$$w(4,2) = \frac{1}{2} L i_L^2(4) - \frac{1}{2} L i_L^2(2)$$

$$w(4,2) = 0 - 0.5 * 10 * 10^{-3} (20 * 10^{-3})^2 \text{ J}$$

THE VALUE IS NEGATIVE BECAUSE THE INDUCTOR IS SUPPLYING ENERGY PREVIOUSLY STORED

The Dual Relationship for Capacitors and Inductors

Capacitor

$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(x) dx + v(t_0)$$

$$p(t) = Cv(t) \frac{dv(t)}{dt}$$

$$w(t) = \frac{1}{2} Cv(t)^2$$

$$C \rightarrow L$$

$$v \rightarrow i$$

$$i \rightarrow v$$

Inductor



$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = \frac{1}{L} \int_{t_0}^t v(x) dx + i(t_0)$$

$$p(t) = Li(t) \frac{di(t)}{dt}$$

$$w(t) = \frac{1}{2} Li^2(t)$$

Condensadores em série

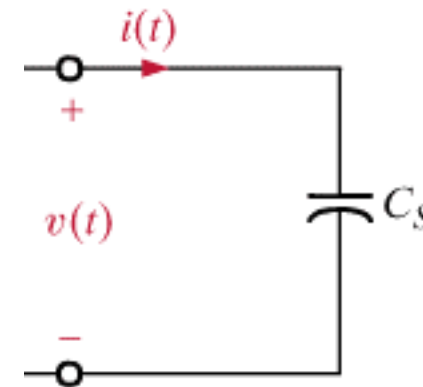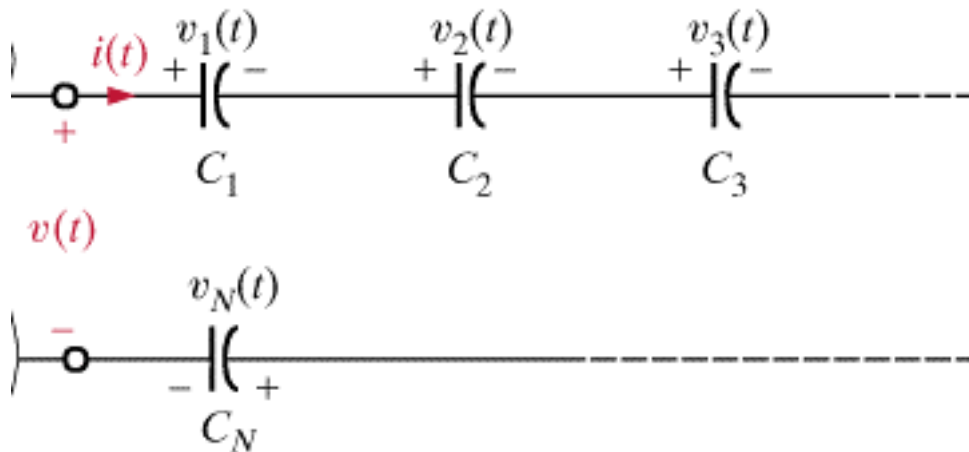

$$v(t) = v_1(t) + v_2(t) + v_3(t) + \dots + v_N(t)$$

$$v_i(t) = \frac{1}{C_i} \int_{t_0}^t i(t) dt + v_i(t_0)$$

$$v(t) = \left(\sum_{i=1}^N \frac{1}{C_i} \right) \int_{t_0}^t i(t) dt + \sum_{i=1}^N v_i(t_0)$$


$$\frac{1}{C_s} = \sum_{i=1}^N \frac{1}{C_i} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$

$$v(t_0) = \sum_{i=1}^N v_i(t_0)$$


Semelhante a resist. Em paralelo

$$C_s = \frac{C_1 C_2}{C_1 + C_2}$$

Combinação serie de 2 condensadores

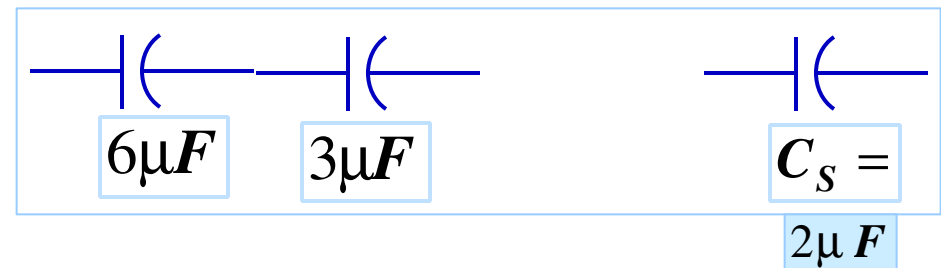

Condensadores em paralelo

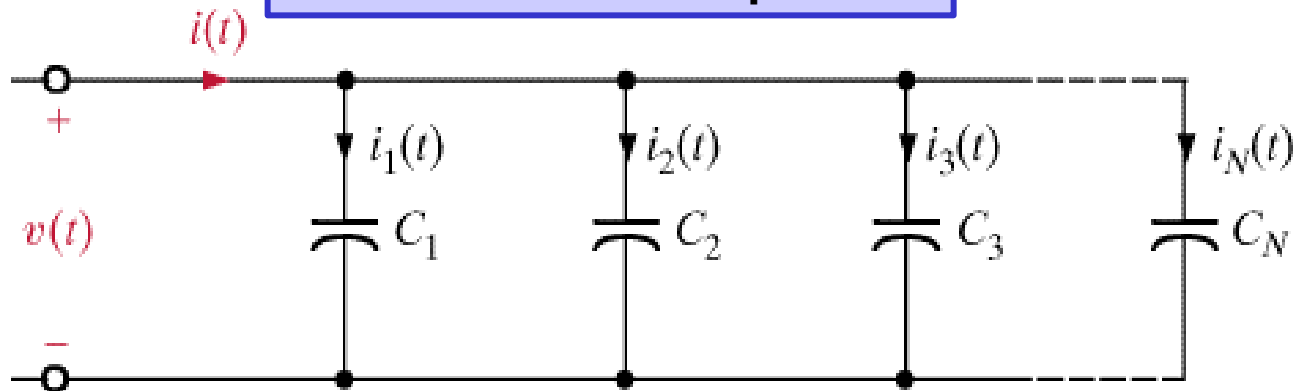


$$i(t) = i_1(t) + i_2(t) + i_3(t) + \dots + i_N(t)$$

$$i_k(t) = C_k \frac{dv}{dt}(t)$$


$$i(t) = C_1 \frac{dv(t)}{dt} + C_2 \frac{dv(t)}{dt} + C_3 \frac{dv(t)}{dt} + \dots + C_N \frac{dv(t)}{dt}$$

$$i(t) = \left(\sum_{i=1}^N C_i \right) \frac{dv(t)}{dt}$$

$$C_p = C_1 + C_2 + C_3 + \dots + C_N$$


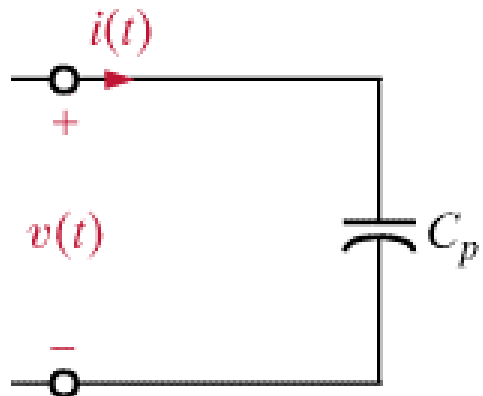


EXEMPLO

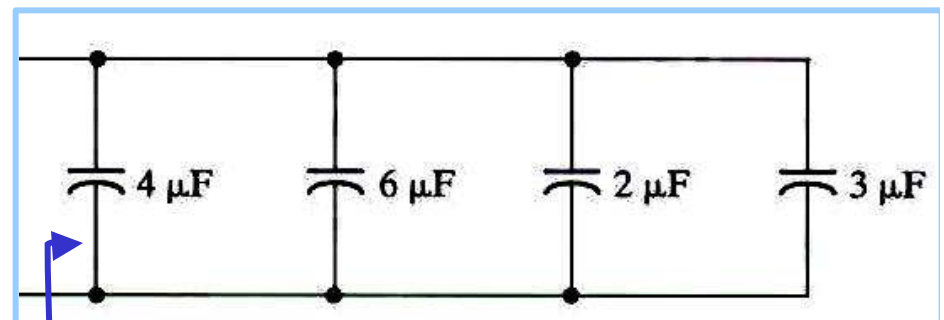


$$C_P = 4 + 6 + 2 + 3 = 15 \mu F$$

EXEMPLO

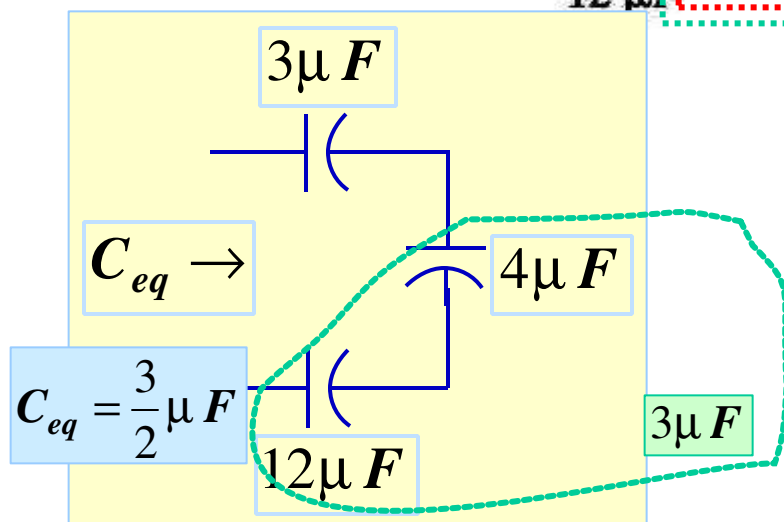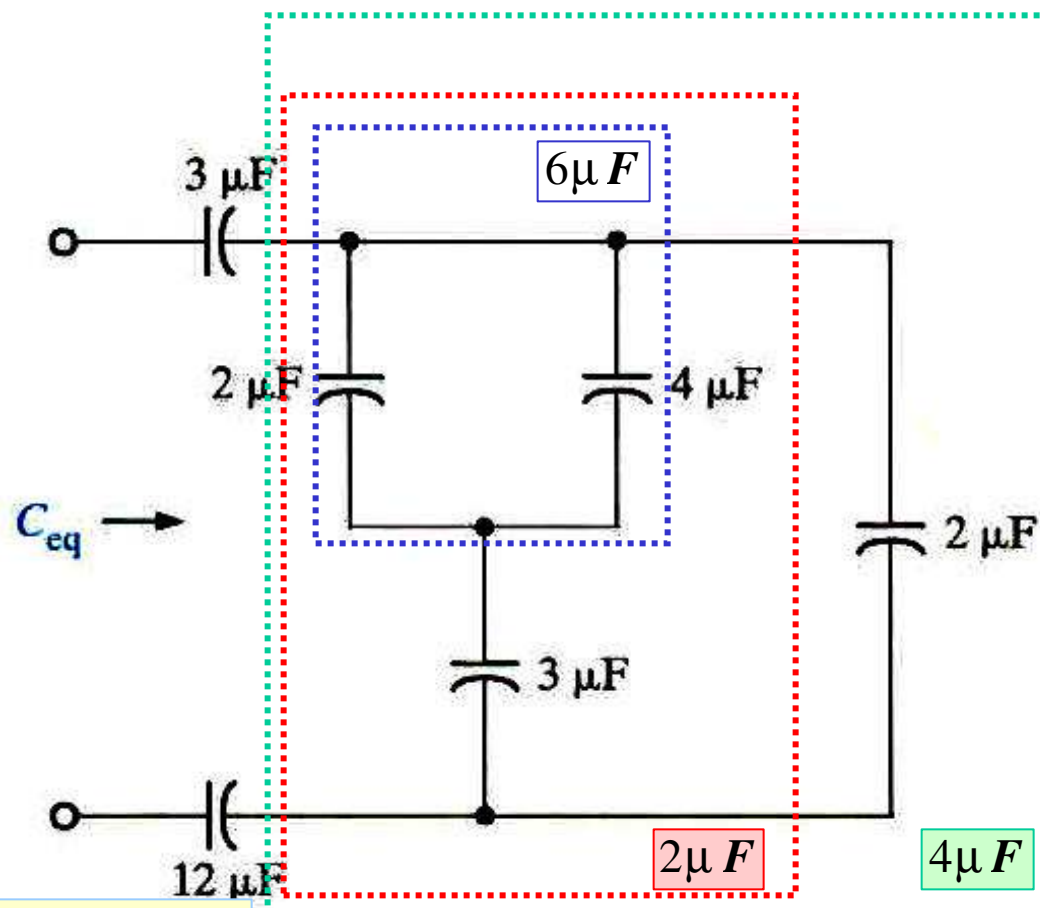

SERIES INDUCTORS

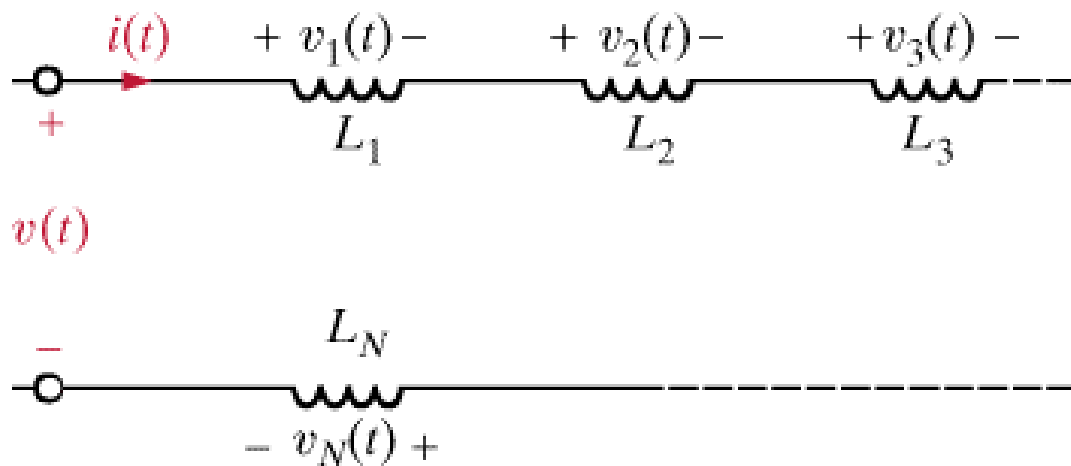


$$v(t) = v_1(t) + v_2(t) + v_3(t) + \dots + v_N(t)$$

$$v_k(t) = L_k \frac{di}{dt}(t)$$


$$\begin{aligned} v(t) &= L_1 \frac{di(t)}{dt} + L_2 \frac{di(t)}{dt} + L_3 \frac{di(t)}{dt} + \dots + L_N \frac{di(t)}{dt} \\ &= \left(\sum_{i=1}^N L_i \right) \frac{di(t)}{dt} \end{aligned}$$

$$L_S = \sum_{i=1}^N L_i$$

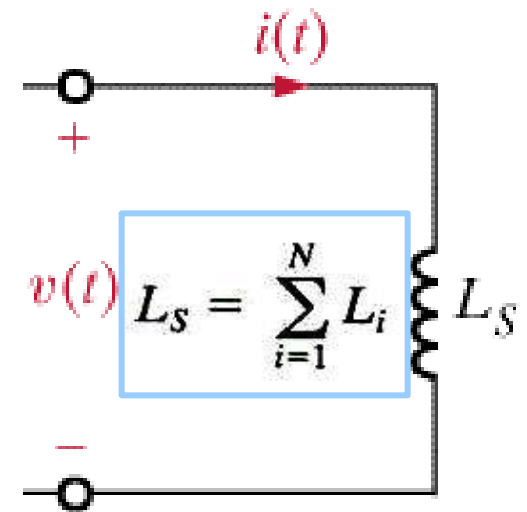


$$v(t) = L_S \frac{di}{dt}(t)$$

LEARNING EXAMPLE

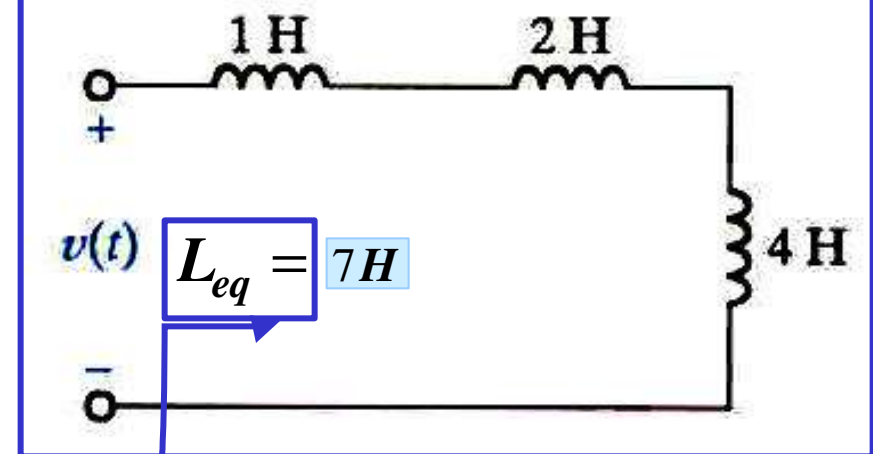

PARALLEL INDUCTORS

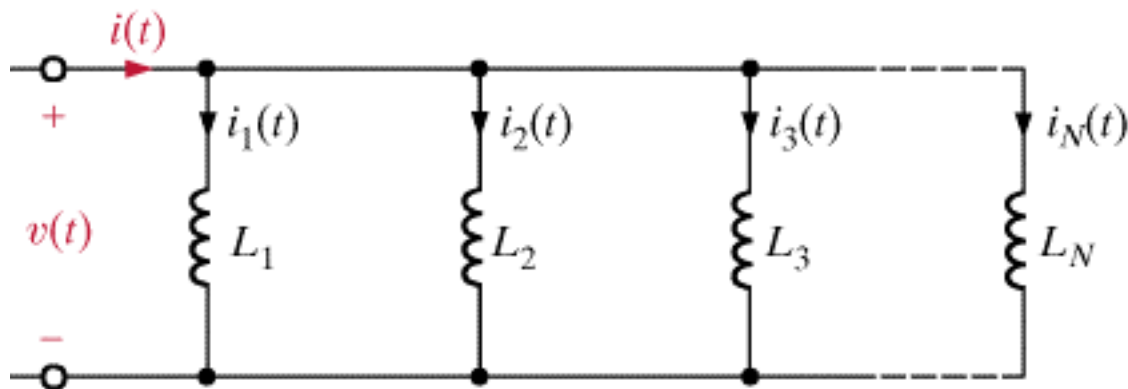

$$i(t) = i_1(t) + i_2(t) + i_3(t) + \dots + i_N(t)$$

$$i_j(t) = \frac{1}{L_j} \int_{t_0}^t v(x) dx + i_j(t_0)$$


$$i(t) = \left(\sum_{j=1}^N \frac{1}{L_j} \right) \int_{t_0}^t v(x) dx + \sum_{j=1}^N i_j(t_0)$$

$$\frac{1}{L_p} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_N}$$

$$i(t_0) = \sum_{j=1}^N i_j(t_0)$$

$$i(t) = \frac{1}{L_p} \int_{t_0}^t v(x) dx + i(t_0)$$

LEARNING EXAMPLE

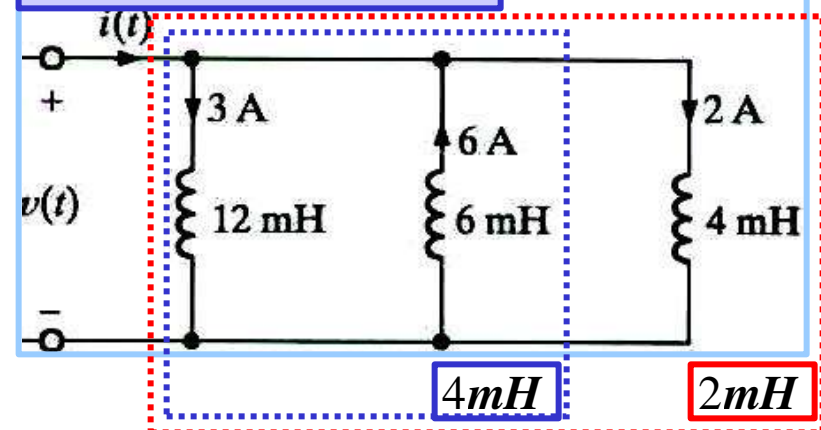

$$i(t_0) = 3A - 6A + 2A = -1A$$

INDUCTORS COMBINE LIKE RESISTORS
CAPACITORS COMBINE LIKE CONDUCTANCES

SUMMARY

- The important (dual) relationships for capacitors and inductors are as follows:

$$q = Cv$$

$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(x) dx$$

$$p(t) = Cv(t) \frac{dv(t)}{dt}$$

$$W_C(t) = 1/2 Cv^2(t)$$

$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(x) dx$$

$$p(t) = Li(t) \frac{di(t)}{dt}$$

$$W_L(t) = 1/2 Li^2(t)$$

- The passive sign convention is used with capacitors and inductors.
- In dc steady state a capacitor looks like an open circuit and an inductor looks like a short circuit.
- Leakage resistance is present in practical capacitors and inductors.
- When capacitors are interconnected, their equivalent capacitance is determined as follows: Capacitors in series combine like resistors in parallel and capacitors in parallel combine like resistors in series.
- When inductors are interconnected, their equivalent inductance is determined as follows: Inductors in series combine like resistors in series and inductors in parallel combine like resistors in parallel.
- RC operational amplifier circuits can be used to differentiate or integrate an electrical signal.




L-C

STOP

RC OPERATIONAL AMPLIFIER CIRCUITS

INTRODUCES TWO VERY IMPORTANT PRACTICAL CIRCUITS
BASED ON OPERATIONAL AMPLIFIERS

THE IDEAL OP-AMP

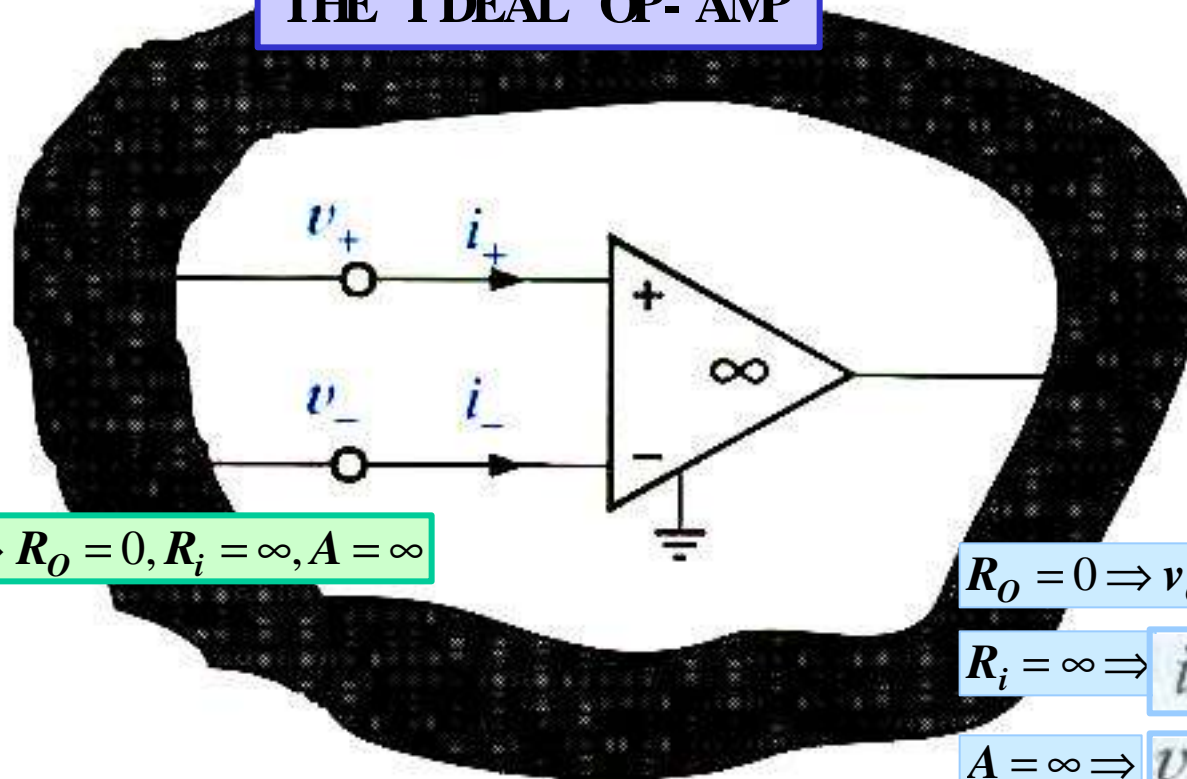


IDEAL $\Rightarrow R_o = 0, R_i = \infty, A = \infty$

$$R_o = 0 \Rightarrow v_o = A(v_+ - v_-)$$

$$R_i = \infty \Rightarrow i_+ = i_- = 0$$

$$A = \infty \Rightarrow v_+ = v_-$$

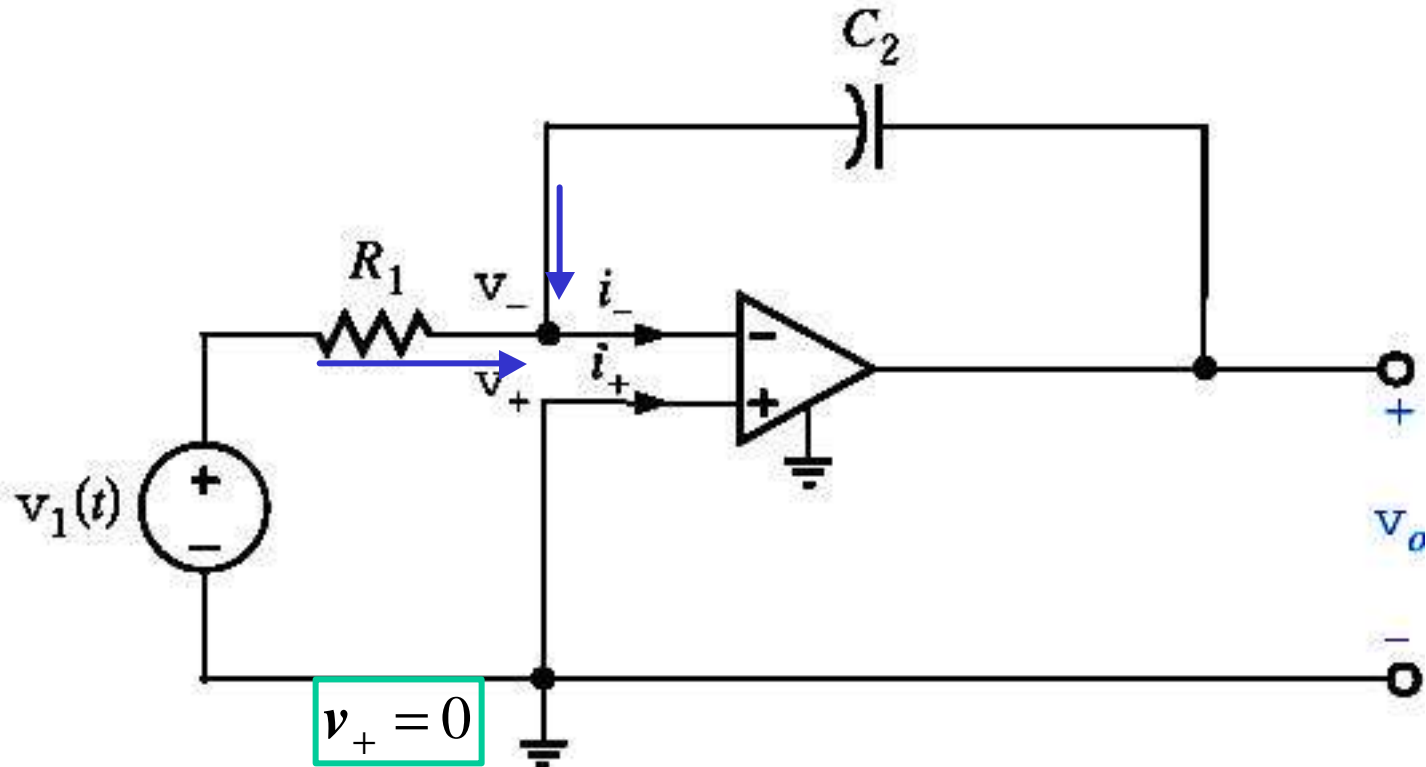RC OPERATIONAL AMPLIFIER CIRCUITS -THE INTEGRATOR



$$\frac{v_1 - v_-}{R_1} + C_2 \frac{d}{dt} (v_o - v_-) = i_-$$


IDEAL OP-AMP ASSUMPTIONS

$$\begin{aligned} v_- &= v_+ \quad (A = \infty) \\ i_- &= 0 \quad (R_i = \infty) \end{aligned}$$

$$\frac{v_1}{R_1} = -C_2 \frac{dv_o}{dt}$$

$$\begin{aligned} v_o(t) &= \frac{-1}{R_1 C_2} \int_{-\infty}^t v_1(x) dx \\ &= \frac{-1}{R_1 C_2} \int_0^t v_1(x) dx + v_o(0) \end{aligned}$$

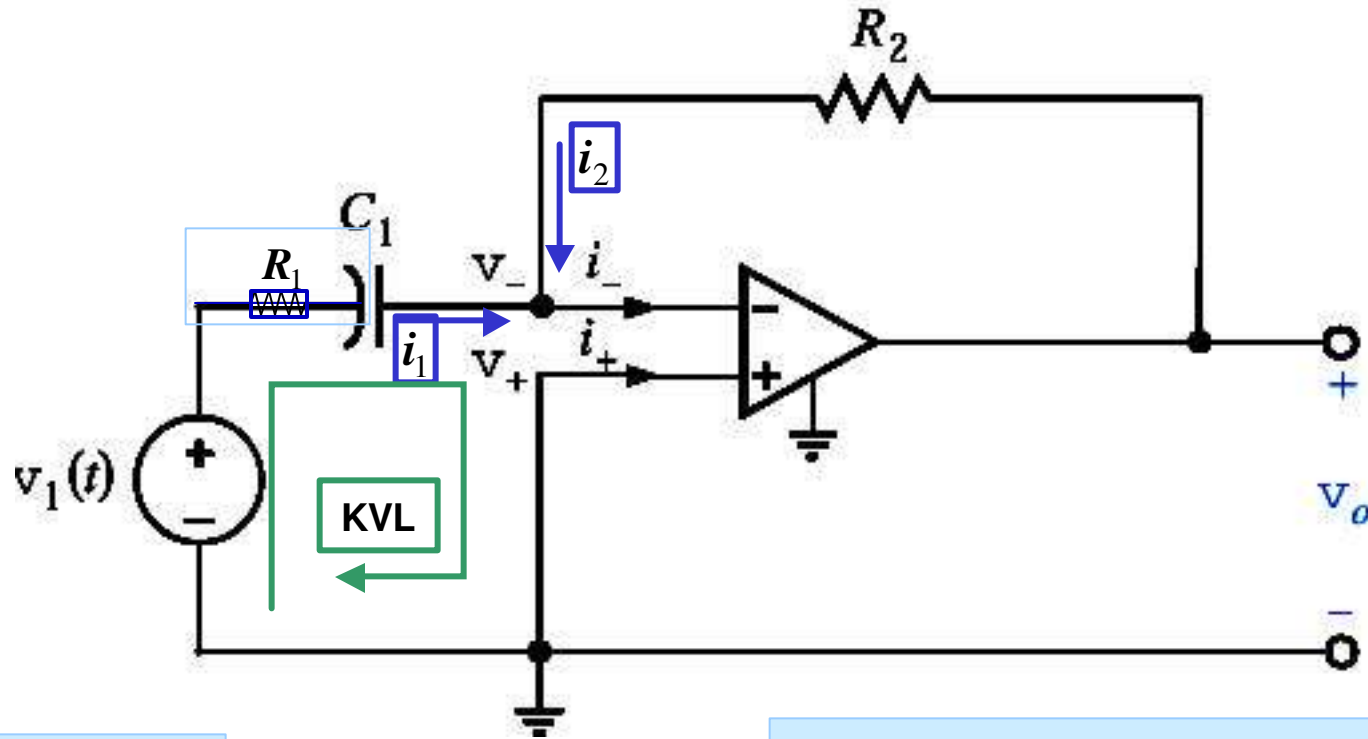RC OPERATIONAL AMPLIFIER CIRCUITS - THE DIFFERENTIATOR



$$v_+ = 0$$

$$\text{KCL@}v_- : i_1 + i_2 = i_-$$

IDEAL OP-AMP ASSUMPTIONS

$$v_- = v_+ \quad (A = \infty)$$

$$i_- = 0 \quad (R_i = \infty)$$

$$\Rightarrow i_1 + \frac{v_o}{R_2} = 0$$

$$v_1(t) = R_1 i_1 + \frac{1}{C_1} \int_{-\infty}^t i_1(x) dx$$

DIFFERENTIATE

$$R_1 C_1 \frac{di_1}{dt} + i_1 = C_1 \frac{dv_1}{dt}(t)$$

$$\text{replace } i_1 \text{ in terms of } v_o \quad (i_1 = -\frac{v_o}{R_2})$$

$$R_1 C_1 \frac{dv_o}{dt} + v_o = -R_2 C_1 \frac{dv_1}{dt}(t)$$

IF R1 COULD BE SET TO ZERO WE WOULD HAVE AN IDEAL DIFFERENTIATOR. IN PRACTICE AN IDEAL DIFFERENTIATOR AMPLIFIES ELECTRIC NOISE AND DOES NOT OPERATE. THE RESISTOR INTRODUCES A FILTERING ACTION. ITS VALUE IS KEPT AS SMALL AS POSSIBLE TO APPROXIMATE A DIFFERENTIATOR



GEAUX